

PRN No. RBT24/E018	Total No. of Questions:
-----------------------	----------------------------

FYMSEEC132411B

JSPM's

Rajarshi Shahu College of Engineering, Tathawade, Pune- 411033

(An Empowered Autonomous Institute Affiliated to Savitribai Phule Pune University)

Examination: Mid Semester Examination (MSE)

Semester: I

Academic Year: 2024-25

Programmes: Electronics and Telecommunication Engineering, Electrical Engineering, Civil Engineering, Information Technology and Computer Science and Business Systems

Examination Class: F. Y. B. Tech.

Course Code: EE1201T Course Name and Pattern: Introduction to Electrical Engineering

Duration: 1.15 Hour

Max. Marks: 30 Marks

1. Solve section All three sections A, B, C
2. Choose and answer **one** option from each question.
3. Assume suitable and necessary data wherever required.
4. Use of log table, scientific calculator, steam table is allowed.

Section A

Q. No.	Question	Bloom's Level	Marks	COs
1	a. Define magnetic flux density with its formula and unit.	BL 1	02	CO1
	b. List the types of induced EMF's in electrical circuit with their formulas.	BL 1	02	CO1
OR				
1	a. Define Relative permeability with its formula and unit.	BL 1	02	CO1
	b. State Faraday's laws of Electromagnetic Induction.	BL 1	02	CO1
2	a. What are the types of transformer based on number of phases and level of voltages?	BL 1	02	CO1
	b. Define time period and frequency with its unit.	BL 1	02	CO1
OR				
2	a. What are the main two parts of transformer? Name the material used for the same.	BL 1	02	CO1
	b. List the different type of powers in single phase AC circuits with their formula and unit.	BL 1	02	CO1
3	Show the ac voltage and current waveforms for purely resistive load and comment on it.	BL 1	02	CO1
OR				
3	Name the types of reactances with their formula and unit.	BL 1	02	CO1

Section B

Q. No.	Question	Bloom's Level	Marks	COs
4	a. Classify the different types of losses in detail with their formulae.	BL 2	03	CO2
	b. Explain the operation of ac circuit with purely capacitive load in terms of circuit diagram, voltage and current equation.	BL 2	03	CO2
OR				
4	a. Derive the expression for resonant frequency with usual notation.	BL 2	03	CO2
	b. Compare electric circuit with magnetic circuit in terms of similarities and dissimilarities.	BL 2	03	CO2
5	a. For pure sinusoidal waveform show that $V_{avg} = \frac{2V_m}{\pi}$.	BL 2	03	CO2
	b. Explain the concept of admittance with its components.	BL 2	03	CO2
OR				
5	a. Explain the concept of capacitive reactance in terms of definition, circuit diagram, formula and unit.	BL 2	03	CO2
	b. Show well labeled circuit for star connected balanced resistive load.	BL 2	03	CO2

Section C

Q. No.	Question	Bloom's Level	Marks	COs
6	a. Show the expression of current flowing in a pure resistor of 40Ω connected across 230V, 50Hz, AC supply with the phasor diagram.	BL 3	04	CO3
	b. A 5 kVA, 5000/1000V, 50Hz, single phase transformer has iron loss of 150 watt and full load copper loss of 180 watt. Estimate efficiency of the transformer at: i. Half load and 0.85 p.f lagging ii. 75 % of the full load and 0.8 power factor leading	BL 3	04	CO3
OR				
6	a. An electric conductor of effective length 5 m is moving with velocity 50 m/s in a magnetic field having density 1.5 T. Estimate EMF induced in a conductor if conductor is moving in a direction (a) 45° (b) 90° with respect to magnetic field.	BL 3	04	CO3
	b. An alternating current is given by $i(t) = 12 \sin 314t$. Compute RMS and average value, frequency, time period of current.	BL 3	04	CO3